

Go to: [Course homepage](#), [Lectures](#)

Lecture: 23 (iq20) Microscopic picture of a circuit

1. A simple circuit: Macro vs micro descriptions
2. Drude model and drift velocity Clicker 23.1
3. Mechanical battery and steady decreasing surface charge density. Clicker 23-2
4. Grading in surface charge density leads to field in the center of the wire. Clicker fig19.19.
5. Steady state of a current flow in a circuit
 - a. One loop: i maintains the same value throughout
 - b. Node: $i_{in} = i_1 + i_2$
6. Examples
 - a. Loop equations and node equations Kirchhoff's rules.
 - b. Simple circuit
 - c. Example with a simple series connection
 - d. Example with a simple parallel connection
 - e. Example with 4 identical bulbs

Announcement:


Midterm 2: Class average is 67.

- Reminder: How to determine the letter grade you made for this midterm?
 - Find your scaled score which is located near the bottom of the grading page.
 - Two letter grades for each exam:
 - letter grade-1 based on % cutoffs.
 - Letter grade-2 based on scaled score cutoffs.
 - The letter grade you have made for this exam is the higher of the two letter grades, if there is a difference.

Redo mt2: Due time this coming Sunday, 11:30pm, 3/10.

ig 20 Electric field + electric current


Single circuit

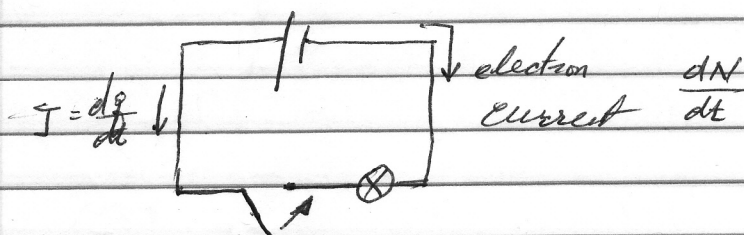

Drift velocity:

$E=0$ Random motion

$E>0$ Steady drift

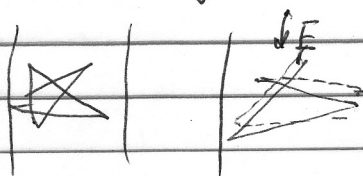

random drift:



$$v = a t_c = \frac{eE}{m} t_c = \left(\frac{e t_c}{m} \right) E = \mu E$$

$v \propto E$

Drift

→ clicker 23.1

μ mobility

Electron number current:

$$i = \frac{dN}{dt} = \frac{n A \Delta L}{\Delta t} = n A v = n A \mu E$$

Drude model: $i = n A \mu E$


clicker 23.2

Surface charge distributions:

Grading is the surface charge distribution

\Rightarrow electric field inside the wire,


• checker 19.19

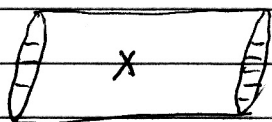

If $i = \text{const} \Rightarrow E = \text{const}$ in the circuit.

\Rightarrow Surface charge distribution with gradient throughout the circuit.

$$i = nA v = nA u E,$$

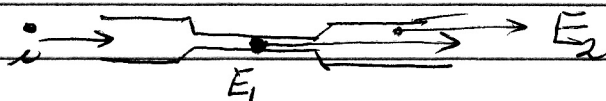

for steady i , with same material $nu = \text{const}$

$$AE = \text{const}.$$

Smaller is A, Bigger is E.


$$\text{If } A_1 \ll A_2 \\ E_1 \gg E_2$$

Solving circuit problems:

Sec 23-3

Given: Battery emf and circuit solve for E & i across each element of the circuit.

Example 1:

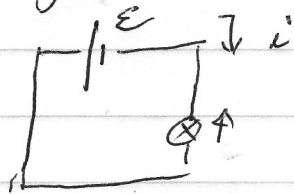


loop eqn:

$$\mathcal{E} - EL = 0, \quad E = \frac{\mathcal{E}}{L} \equiv E_0$$

$$i = nA v = nA u E = nA u \frac{\mathcal{E}}{L} \equiv i_0$$

Example 2:

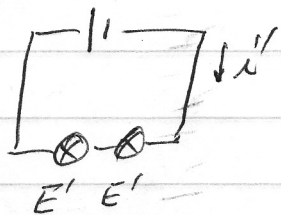


$$\mathcal{E} - E'L - E'L = 0$$

$$\therefore E' = \frac{\mathcal{E}}{2L} = \frac{E_0}{2}$$

$$i' = nA u E' = nA u \frac{\mathcal{E}}{2L} = \frac{i_0}{2}$$

$$\therefore E' = \frac{E_0}{2}, \text{ and } i' = \frac{i_0}{2}$$

Example 3:

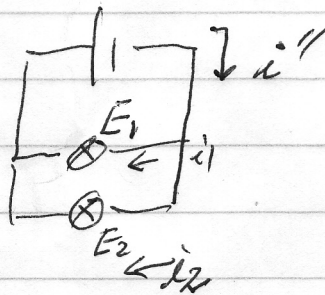

$$\mathcal{E} - E_1 L = 0$$


$$\mathcal{E} - E_2 L = 0$$

$$i_1 = nA u E_1 = nA u \frac{\mathcal{E}}{L} = i_0$$

$$i_2 = i_0$$

$$\therefore i'' = 2i_0, \quad E_1 = E_2 = E_0$$

Example 4

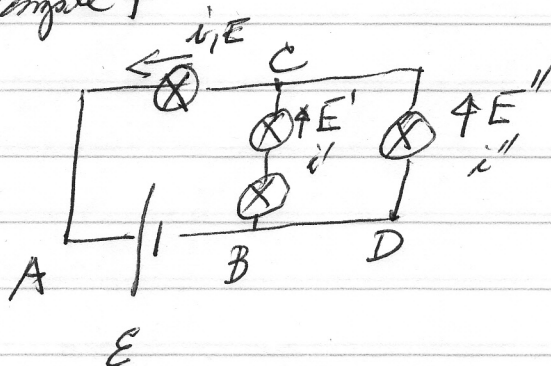

$$ABCA: \mathcal{E} - 2E'L - EL = 0 \quad (1)$$

$$ABDCA: \mathcal{E} - E'L - EL = 0 \quad (2)$$

$$\text{Node eqn: } i = i' + i'' \quad (3)$$

$$\begin{cases} i = nA\omega E \\ i' = nA\omega E' \\ i'' = nA\omega E'' \end{cases} \quad \therefore \text{Node eqn} \Rightarrow E = E' + E'' \quad (4)$$

3 eqns + 3 unknowns.

Solve for E', E'', E Express all E 's in terms of E''

$$2E' = E'', \quad E' = \frac{E''}{2}$$

$$E = E' + E'' = \frac{3}{2}E''$$

$$(1): \mathcal{E} - E''L - \frac{3}{2}E''L = \mathcal{E} - \frac{5}{2}E''L = 0, \quad E'' = \frac{2\mathcal{E}}{5L}$$

$$E' = \frac{E''}{2} = \frac{1}{5} \frac{\mathcal{E}}{L}, \quad E = E' + E'' = \frac{3}{2}E'' = \frac{3}{5} \frac{\mathcal{E}}{L}.$$