

Go to: [Course homepage](#), [Lectures](#)

## Lecture: 24 (iq21) Ch19 (review), and first part of Ch20

### 1. Selected hw-problems in Ch19-h1

- a. 002
- b. 009 (notice that only 3 compasses illustrated will be considered in the problem)
- c. 013: Surface charge distribution of a circuit with a battery and two resistors, where  $R_1 \gg R_2$ .
- d. 014, 015 selected choices in these two questions will be discussed.

### 2. Selected topics related to Ch20-h1



- a. Ohm's law:
  - Ohm's law-I (without specification on dimensions):  $J = \sigma E$ , where  $\sigma = |q|/\nu$ , the conductivity of the matter.
  - Ohm's law II (with dimensions):  $V = IR$ ,  $R = \rho l/A$ ,  $\rho$  is the resistivity.
- b. 002
- c. 003
- d. 017, 18 spherical capacitor
- e. Time dependence of RC circuit.

## Announcement:

Midterm 2: Class average is 67.

- Reminder: How to determine the letter grade you made for this midterm?
  - Find your scaled score which is located near the bottom of the grading page.
  - Two letter grades for each exam:
    - letter grade-1 based on % cutoffs.
    - Letter grade-2 based on scaled score cutoffs.
  - The letter grade you have made for this exam is the higher of the two letter grades, if there is a difference.
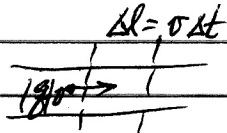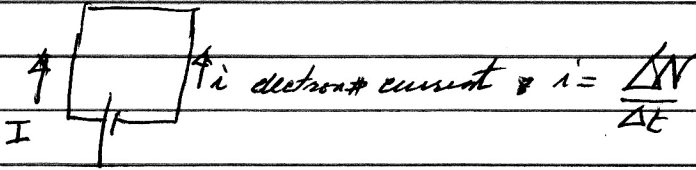
# Ch 19-11 Microscopic description of a current




check pt

$$n, A, v, \Delta t$$

$$\Delta N = n A \Delta L = n A v \Delta t$$

$$\therefore \frac{\Delta N}{\Delta t} = n A v$$

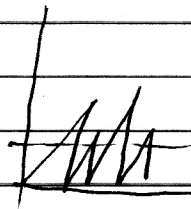Drude model: Taking into account collisions along the way,



$$\bar{v} = a \bar{t}_c = \frac{e E}{m} \bar{t}_c = \left( \frac{e \bar{t}_c}{m} \right) E$$

$$\text{Since } |\bar{v}_{\text{thermal}}| \gg |\bar{v}_{\text{drift}}|$$

$$\frac{3}{10^4} \text{ s}$$


$$\sim 0.1 \text{ m/s}$$

$$\bar{t}_c = \frac{|\bar{h}|}{|\bar{v}_{\text{th}} + \bar{v}_{\text{drift}}|} \sim \frac{|\bar{h}|}{|\bar{v}_{\text{th}}|} = \text{const at a given temp.}$$

$$\bar{v} = \mu E$$

mobility

Ch 19-11-002

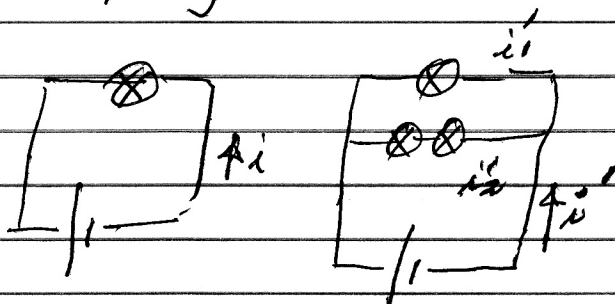

Compare  $i'$  with  $i$ :  $E_1 L = \mathcal{E}$   
 $E L = \mathcal{E}$

$\therefore E_1' = E$ , or for identical bulbe  $i_1' = i$

$$n A_1 E_1' = n A_1 \frac{\mathcal{E}}{L} = n A_1 E$$


Compare  $i_2'$  vs  $i$

Loop ABCA  $\mathcal{E} - 2E_2' L = 0$

$$E_2' = \frac{\mathcal{E}}{2L}, \quad E_2' = \frac{E}{2}, \quad \text{or } i_2' = \frac{i}{2}$$

Compare  $i'$  with  $i$ ,  $i' = i_1 + i_2 = i + \frac{i}{2} = \frac{3i}{2}$

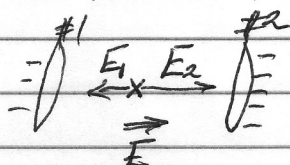
Ch19-h1-013 Phys: Change of local surface charge density leads to the local  $E$  within the wire



Inspection on wrong choices:


6  $\frac{+/-}{+/+}$  Wrong sign should be  $\frac{+/-}{-/-}$

3  $R_1 = 25 \Omega, R_2 = 5 \Omega$

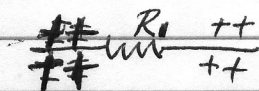


$$\Delta V_1 = I R_1$$

$$\Delta V_2 = I R_2$$

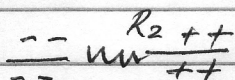

Picture has smaller charge density  
 Change across  $R_1$ . So  $\Delta V_1 < \Delta V_2$


This contradicts to  $R_1 > R_2$

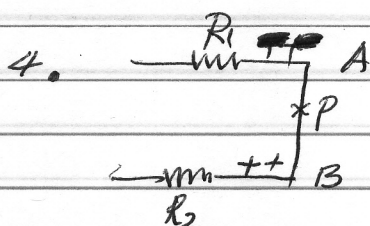

Current flow should be clockwise,  
i.e. from A to B, or at P,  $\mathbf{I}$  is downwards,  
or  $E_p$  is downward.

The surface charge leads to  $E_p$  <sup>surface</sup> upward  
which is inconsistent with CW current flow.

3. Surface charge distribution implies

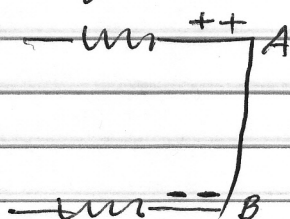

There is a potential difference  
between A & B.

This ~~contradiction~~ is inconsistent with  
~~the~~ set-up where

$V_A - V_B$  across a wire should have  $\Delta V = 0$ .

Ch19-h1-14.

choices 1. Incorrect. In the steady flow circuit  $i = \text{const}$ ,  $E = \text{const}$   
but  $E \neq 0$ .

2. At G and at C, the cross section is the same  
 $i_G = n A_G u E_G$ ,  $i_C = n A_C u E_C$ . So  $i_G = i_C$  implies  
 $E_G = E_C$ .

3. Correct by inspection

4. Incorrect. We need excess charge to  
generate  $E$ , in turn the current in the wire.



CH19-RI 015.

Steady

1. Correct. Here  $i_E = i_D = i_C$  (flows within 1 loop)

$$i_E = n A_E u E_C$$

$$i_D = n A_D u E_D$$

$$\therefore A_E E_C = A_D E_D, \quad E_D = \frac{A_E E_C}{A_D}$$

Since  $E_D$  is much bigger, local surface charge gradient must be larger also.

2. Yes. There is a steady current flows.

The electron current is the same throughout the current loop.

Purvis on chap 20.

Ohm's Law Conventional "macroscopic" Ohm's Law are,

Ohm's Law-1:  $J = \sigma E$  (1) where  $\sigma$  is the conductivity

Ohm's Law-2:  $V = IR$  (2)

How are they related to  $i = n A u E$ ?

Define  $I = |q| i = |q| n A u E$ .

So  $J = \frac{I}{A} = |q| n u E$ .

3.  $\sigma = |q| n u$ .

Ohm's Law II follows from:

$$E = \frac{V}{L} = \frac{1}{\sigma} J = \frac{\rho}{\sigma} \frac{I}{A},$$

$$\text{or } V = \left( \frac{\rho L}{A} \right) I$$

$$= RI, \text{ where } R = \frac{\rho L}{A} \text{ is used.}$$