


Go to: [Course homepage](#), [Lectures](#)

Lecture: 25 (iq22) Ch20 Circuit elements

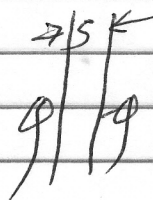1. Capacitor and capacitance:
 - a. Spherical capacitor: large r , $s \ll r$ limit
 - b. One sphere capacitor
2. Energy density: Fill the gap with dielectric medium. $E' = E/K$.
 - a. Case 1: Fixed Q case
 - b. Case 2: Fixed V case. (see the figure)
3. RC circuit: Charging case.
4. An exercise which involves a one capacitor system and a connected two capacitor system.
5. Ohm's law, and power dissipated in a resistor.
6. An exercise on Ohm's laws.


ig 22
Circuit elements

Capacitors: 11-plate we have discussed earlier.



$$C = \frac{Q}{V} = \frac{Q}{Es} = \frac{\epsilon_0 A}{s} \frac{Q}{Q/A} = \frac{\epsilon_0 A}{s}$$

Spherical capacitor:

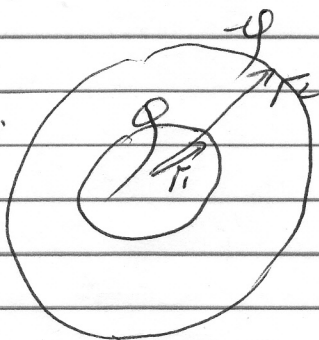

$$V = \Delta V = \frac{kQ}{r_1} - \frac{kQ}{r_2}$$

$$C = \frac{Q}{V} = \frac{1}{\frac{k}{r_1} - \frac{k}{r_2}} \quad (\text{see fig})$$


Long r , $s \ll r$. $r_1 = r$, $r_2 = r + s$

$$C = \frac{1}{\left(\frac{k}{r}\right) \left(1 - \frac{1}{1+s/r}\right)} \approx \frac{1}{\frac{k s}{r^2}} \approx \frac{4\pi r^2 \epsilon_0}{s} = \frac{A \epsilon_0}{s}$$

(Same as 11-plate)

1 sphere capacitor:

$$C = 4\pi \epsilon_0 r$$

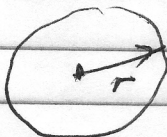

Energy stored:

$$Q = CV$$

$$\Delta q \left(\frac{V}{q} \right) = \frac{V}{q + \Delta q}$$

$$\int_0^Q \Delta U = V \Delta q = \int_0^Q \frac{V}{1 - \frac{\Delta q}{C}} = \frac{Q^2}{2C} = \frac{1}{2} CV^2$$

Energy density: $u = \frac{U}{A_s} \Rightarrow U = \frac{1}{2} \frac{A_s}{s} \epsilon E^2$


$$= \frac{1}{2} \epsilon (A_s) E^2$$

$$\infty U = \frac{U}{A_s} = \frac{1}{2} \epsilon E^2$$

Insert dielectric in the gap: $C' = \frac{Q}{V'} = \frac{Q}{\frac{V}{K}} = KC$

Fix Q case: $U' = \frac{Q^2}{2C'} = \frac{U}{K}$


Fixed V case: $u' = \frac{1}{2} C' V^2 = K U$ (HW) \leftarrow See fig ✓

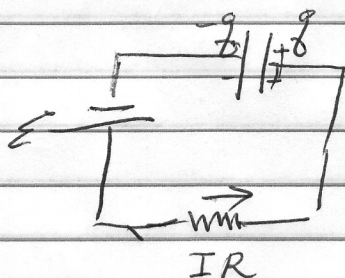RC circuit:Loop eqn: $\Delta V = 0$

$$\mathcal{E} - IR - \frac{q}{C} = 0$$


$t=0^+$: $q=0$, $I = \frac{\mathcal{E}}{R}$

$t=\infty$: $I=0$, $q = \mathcal{E}C$

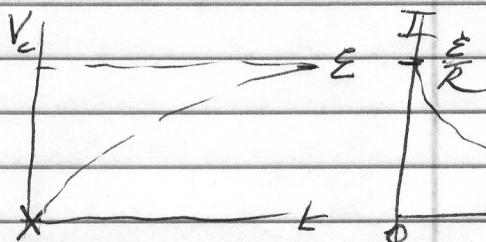

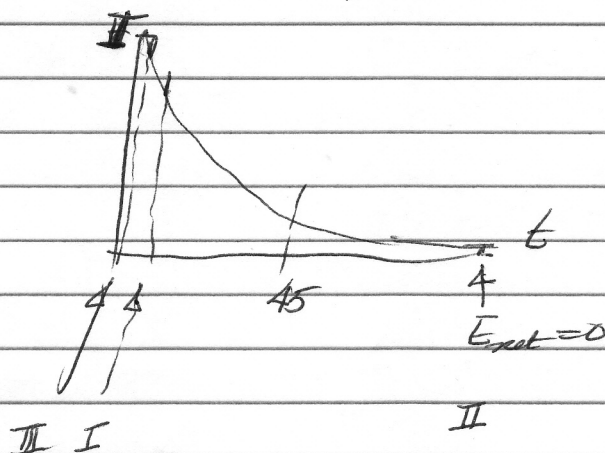Question:

After 45 sec, it gas out
choose diagrams represent 0.01 s, 85 246 s



Choices: 1) I, II, III

2) III, I, II

3) III, II, I

4) II, II, I

Setup:

Case 1 $\frac{Q_0, V_0}{C_0}$

Case 2 $\frac{Q' \text{ } Q''}{V_1 \text{ } C_0 \text{ } V_1 \text{ } C_1}$ $Q' + Q'' = Q_0$

Given: C_0, C_1, V_1

Find: V_0

Hint: $V_0 = \frac{Q_0}{C_0} = \frac{Q' + Q''}{C_0}$

2. Need Q', Q''

But $Q'' = C_1 V_1$. Proceed to find Q' , then V_0

Ohm's Law (OL)

Two versions: OL-1: $J = \sigma E$ (dimension of resistor does not enter)
or $E = \rho J$

OL-2: $V = IR$

micro- $i = nAueE$, $T = 1/q/e$

$$J = \frac{I}{A} = \frac{1/q/nAueE}{A} = \sigma E, \quad \sigma = 1/q/nue$$

$$\text{or } E = \rho J$$

$$\text{OL2: } \frac{V}{L} = \rho \frac{I}{A}, \quad V = \left(\frac{\rho L}{A}\right) I = IR, \quad R = \frac{\rho L}{A}$$

Brightness of light bulb — Power

$$P = \frac{(1/2) V^2}{R} = IV = I^2 R = \frac{V^2}{R}$$

Cut a wire into n equal segments

then make $||$ connection

$$\begin{aligned} L' &\Rightarrow \frac{L}{n} & \therefore R' &= \rho \frac{L'}{A'} = \rho \left(\frac{L}{n}\right) \left(\frac{1}{nA}\right) \\ A' &\Rightarrow nA & &= \left(\frac{\rho L}{A}\right) \frac{1}{n^2} = \frac{R}{n^2} \end{aligned}$$