

## Lecture 26 iq23

### 1. Ohm's Law dissipated in (OL)

- OL-1:  $J = \sigma E$ ,  $E = \rho J$
- OL-2:  $V = IR$
- Series:  $R = R_1 + R_2 + \dots$
- Parallel:  $1/R = 1/R_1 + 1/R_2 + \dots$


### 2. Comments on selected homework in Ch20-h1.

- 002 A circuit with 3 identical bulbs
- 008 A wire across a bulb
- 012 Power dissipated in series case vs in parallel case.

Le26-1

Ohm's Law (OL)

OL-1:

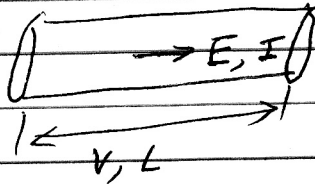

$$V = EL, \text{ current density: } J = \frac{I}{A}$$


$$J = \sigma E$$

Micro:  $i = nA\mu E, I = |q|i$

$$J = \frac{|q|i}{A} = \frac{|q|nA\mu E}{A} = \sigma E, \sigma = |q|n\mu$$

Resistivity:  $E = \frac{J}{\sigma} = \rho J$

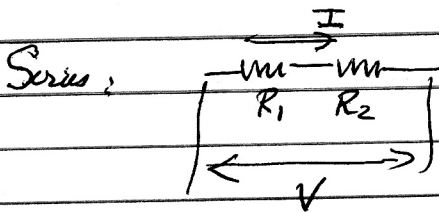OL:  $\frac{V}{L} = \rho \frac{I}{A}, V = \left(\frac{\rho L}{A}\right) I = RI, R = \frac{\rho L}{A}$




$$V = IR_2$$

$$V = V_1 + V_2$$

$$= IR_1 + IR_2$$
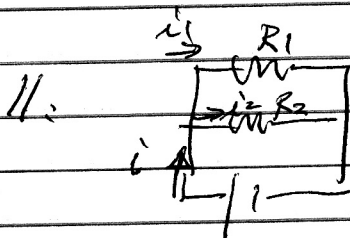
$$\therefore R_{12}^{series} = R_1 + R_2$$




$$i = i_1 + i_2$$

$$\frac{V}{R} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

26-2

Example: 20kt-002

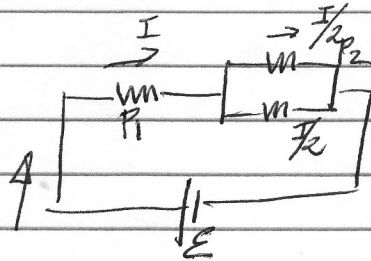


Identical bulbs with  $R$ .

Parallel connection —  $\frac{1}{R_2} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{2}{R}$

$$\therefore R_2 = \frac{R}{2}$$

Interpretation:  $R = \frac{\rho L}{A}$

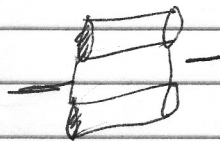


Double area

$$A' = 2A \quad R' = \frac{\rho L}{A'} = \frac{\rho L}{2A} = \frac{R}{2}$$

$$R_{\text{eff}} = R + \frac{R}{2} \rightarrow R_{23} = R + R_{23} = R + \frac{R}{2} = \frac{3}{2}R$$
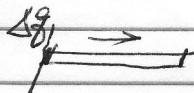
$$\therefore I = \frac{\mathcal{E}}{\left(\frac{3}{2}R\right)}$$




Brightness - Power

$$P = \frac{(\mathcal{E})^2}{R} = IV = I^2 R$$


Compare brightness:  $P_1 = I^2 R = \left(\frac{2}{3} \frac{\mathcal{E}}{R}\right)^2 R = \frac{4}{9} \frac{\mathcal{E}^2}{R}$
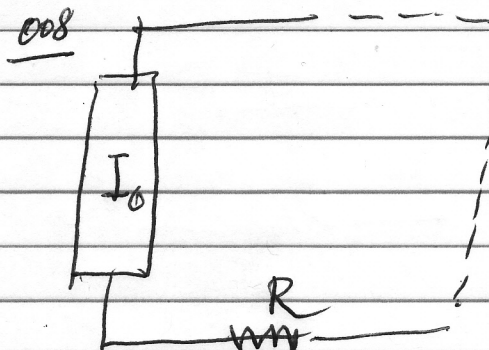
$$P_2 = \left(\frac{I}{2}\right)^2 R = \frac{1}{9} \frac{\mathcal{E}^2}{R}$$



What happens when you  
"short" a resistor?

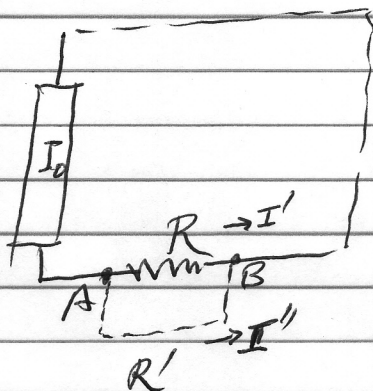Given:  $R$  is the resistor of a  
light bulb.



What happens when  $R' \ll R$   
is connected to the two terminals  
of this bulb?



Hint:  $I_0 = I' + I''$

$$V_A - V_B = I'R + I''R'$$

$$\therefore I' = I'' \left( \frac{R'}{R} \right)$$

$$I_0 = I' \frac{R'}{R} + I'' \approx I''$$

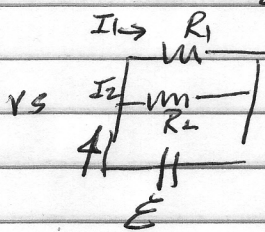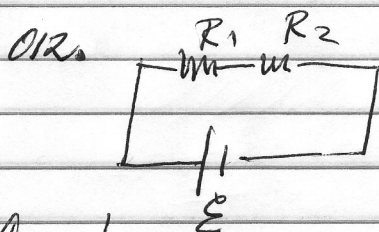So with the wire connected  $I' \approx 0$ . The bulb turns dark  
 $I'' \approx I_0$



Comment:

Case I.  $\mathcal{E} - IR_1 - IR_2 = 0$ ,  $\therefore I\mathcal{E} = I^2 R_1 + I^2 R_2$

$\therefore$  Power delivered by the battery is the power consumed by the bulbs.

Check:  $I\mathcal{E} \stackrel{?}{=} I_1^2 R_1 + I_2^2 R_2$

Again: Power delivered  
= Power consumed

$$RHS = I_1 \mathcal{E} + I_2 \mathcal{E} = (I_1 + I_2) \mathcal{E} = I\mathcal{E}$$